

GATE:IN-42-2023

EE23BTECH11025 - Anantha Krishnan

I. QUESTION

In the circuit shown, the initial binary content of shift register A is 1101 and that of shift register B is 1010. The shift registers are positive-edge triggered, and the gates have no delay.

When the shift control is high, what will be the binary content of the shift registers A and B after four clock pulses?

- (A) $A = 1101, B = 1101$
- (B) $A = 1110, B = 1001$
- (C) $A = 0101, B = 1101$
- (D) $A = 1010, B = 1111$

II. SOLUTION

Code for implementation through Verilog onto FPGA. [write link here](#)